



# Viewer License Agreement

## You Must Read This License Agreement Before Proceeding.

This Scroll Wrap License is the Equivalent of a Shrink Wrap ⇒ Click License,  
A Non-Disclosure Agreement that Creates a "Cone of Silence".

By viewing this Document you **Permanently Release All Rights** that would allow you to restrict the **Royalty Free Use** by anyone implementing in Hardware, Software and/or other Methods in whole or in part what is Defined and Originates here in this Document. This Agreement particularly **Enjoins** the viewer from: Filing any **Patents** (À La Submarine) on said **Technology & Claims** and/or the use of any **Restrictive Instrument** that prevents anyone from using said **Technology & Claims** Royalty Free and without any Restrictions. This also applies to filing any **Trademarks** including but not limited to those being marked with "™" that Originate within this Document. **Trademarks** that Originate here belong to the **Author** of this Document unless otherwise noted. Transferring said **Technology** and/or **Claims** defined here without this Agreement to another Entity for the purpose of but not limited to allowing that Entity to circumvent this Agreement is Forbidden and will NOT release the Entity or the Transfer-er from Liability. Failure to Comply with this Agreement is **NOT** an Option if access to this content is desired. This Document contains **Technology & Claims** that are a **Trade Secret: Proprietary & Confidential** and cannot be transferred to another Entity without that Entity agreeing to this "Non-Disclosure Cone of Silence" **V.L.A.** Wrapper. Combining other Technology with said **Technology** and/or **Claims** is an acknowledgment by the Viewer that [s]he is automatically placing other Technology under the Licenses listed below making this License Self-Enforcing under an agreement of Confidentiality protected by this Wrapper.

The contents of/and this Document are released under following licenses so long as this Agreement remains attached to any and all files, papers, etc... that contain any said **Technology** and/or **Claims**. Any Hardware manufactured with said **Technology** and/or **Claims** must contain a brief message, e.g. "**V.L.A.** This Hardware contains Technology and/or Claims that are Licensed for Unrestricted and Royalty Free Use. Any knowledge gained by viewing this hardware design may not be used to interfere with the manufacture, sale and use of this hardware".

Software only: [GNU General Public License 3.0 \(GPL\)](#)


Hardware (w/ || w/o software): Tucson Arizona Packet Radio TAPR [PDF](#) [ODT](#) [TXT](#)

This Document: [Creative Commons \(CC-BY\)](#)


Scrolling past this **1<sup>st</sup>** page is **The Point of No Return** and Acknowledges that You have Agreed to the Terms above. If you are Unable or Unwilling to Agree to these Terms then Close this Document.

*Magic  
Box*



*Super  
AM*

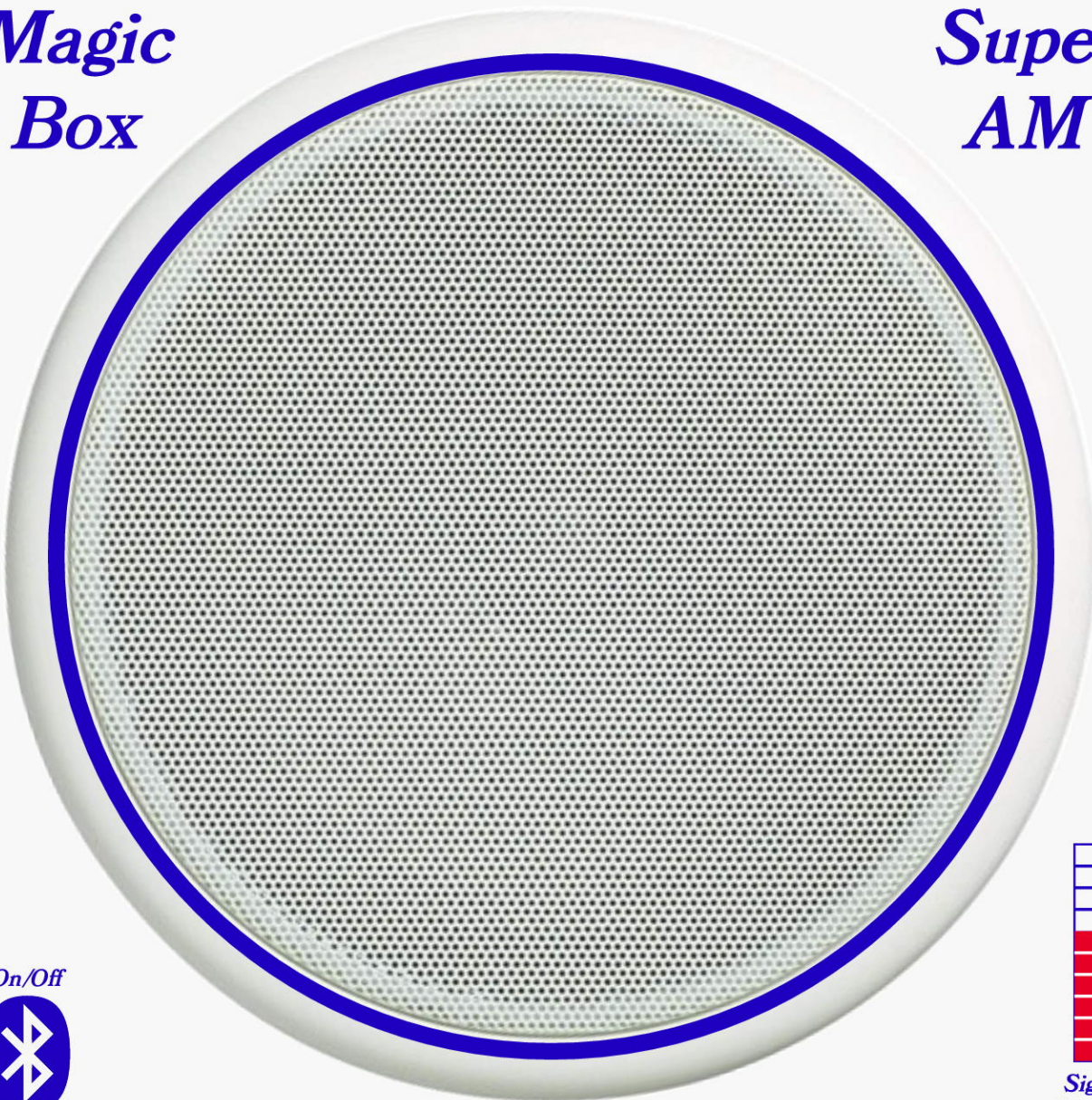

*On/Off*

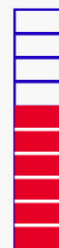

*Signal  
Strength*

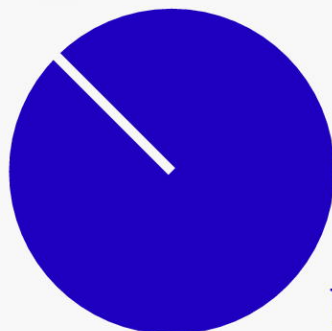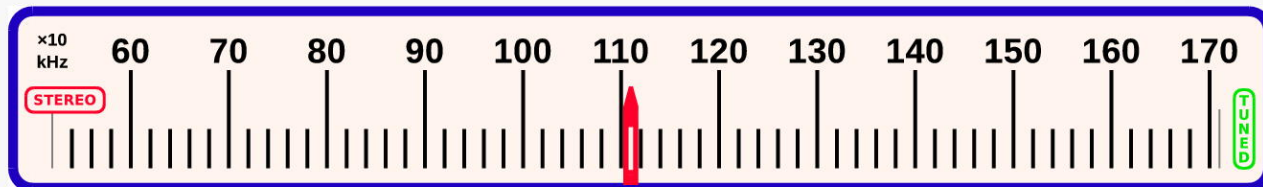

*Volume*  
Loudness Pull



*Bass*  
Low Filter Pull


*Local  
/DX*



10kHz Notch Pull



*Treble*  
High Filter Pull

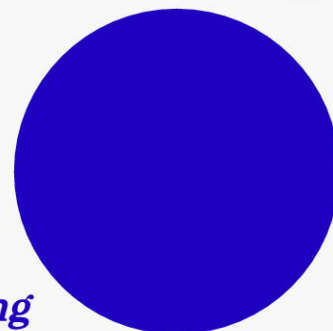

*Tuning*

# MagicBox™

## Super AM

Box O.D. 8"H×6"W×6"D

Inside Volume 225in<sup>3</sup>

¼" Dense MDF

(Formaldehyde Free)

2 Ports @100Hz


¾" dia. PVC/20

5½cm Long, 2.35cm I.D.



-3@84, 0dB@100, +2½@150

To the left is most of the schematic. The antenna is a ferrite loop stick and the coil should be wound over most of the rod with Litz wire to maximize Q, and preferably basket woven. Hopefully the Q will be high in the  $\pm 5\text{kHz}$  range and stay fairly constant across the tuning range. This should be high enough for good selection and image rejection on DX signals. For strong signals De-Qing the antenna to  $\pm 12\frac{1}{2}\text{kHz}$  with a series resistor on the tank will reduce image rejection performance but this is a minimum issue with good signal strength during daytime hours. At wide bandwidth / minimum Q the response should be fairly flat out to  $\pm 10\text{kHz}$  and down to -3dB at  $\pm 12\frac{1}{2}\text{kHz}$  max. A user adjustable pot of 100ΩA provides variable Local/DX Bandwidth/Selectivity.

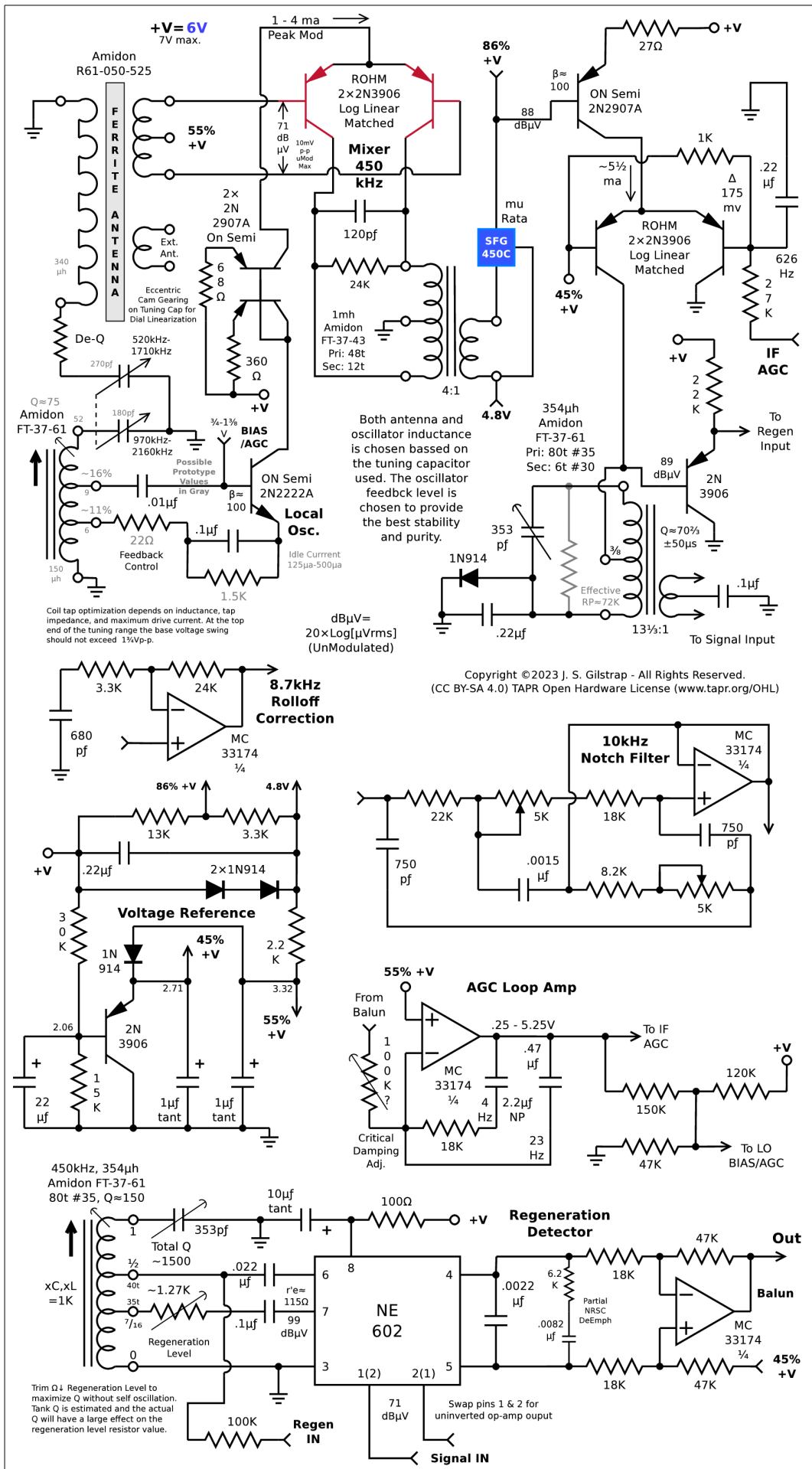The input stage is a differential pair and unlike a single transistor in which its max input level is 60dBμV a differential pair can handle 74dBμV before distorting, 29mVp-p max imum modulation, that's a 14dB advantage. Like a single input transistor it is also the mixer but not the oscillator. Oscillator input is fed into the emitters but is balanced balanced so it






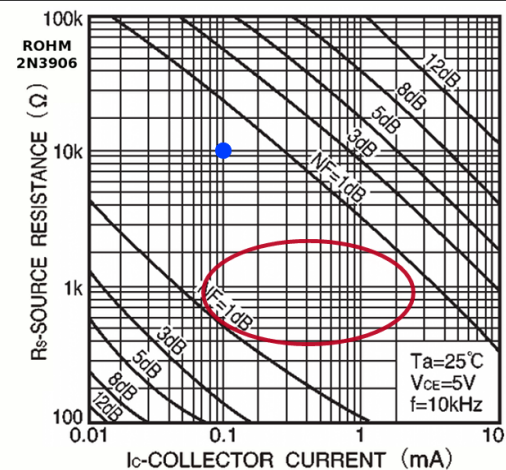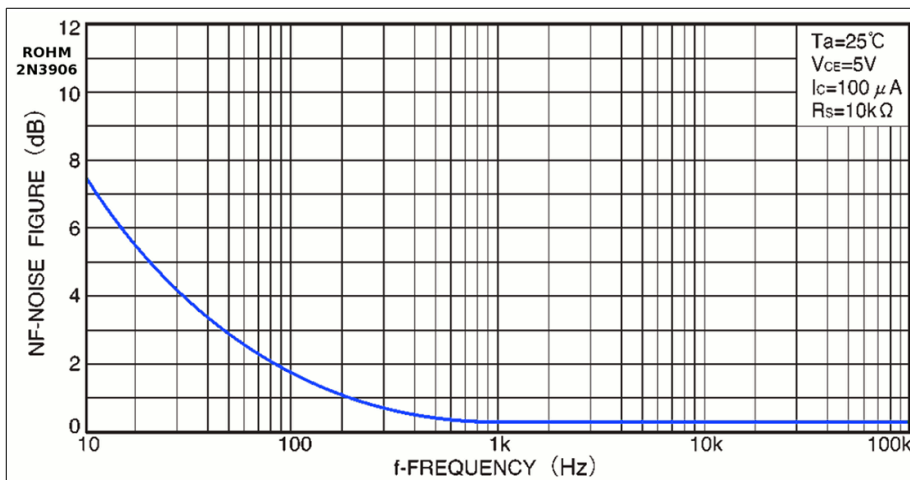


does not appear in the output, only RF & IF which are at a much lower level than the oscillator level. A 2N3906 has a good but not impressive Noise Figure but the **ROHM** units do with a  $\frac{1}{2}$ dB NF starting at 1kHz and extends to 100kHz, as shown above. If this continues for another  $1\frac{1}{2}$  decade then this is probably the best you can get compared to most other transistors. The **RED** oval is the region where it will mostly operate.

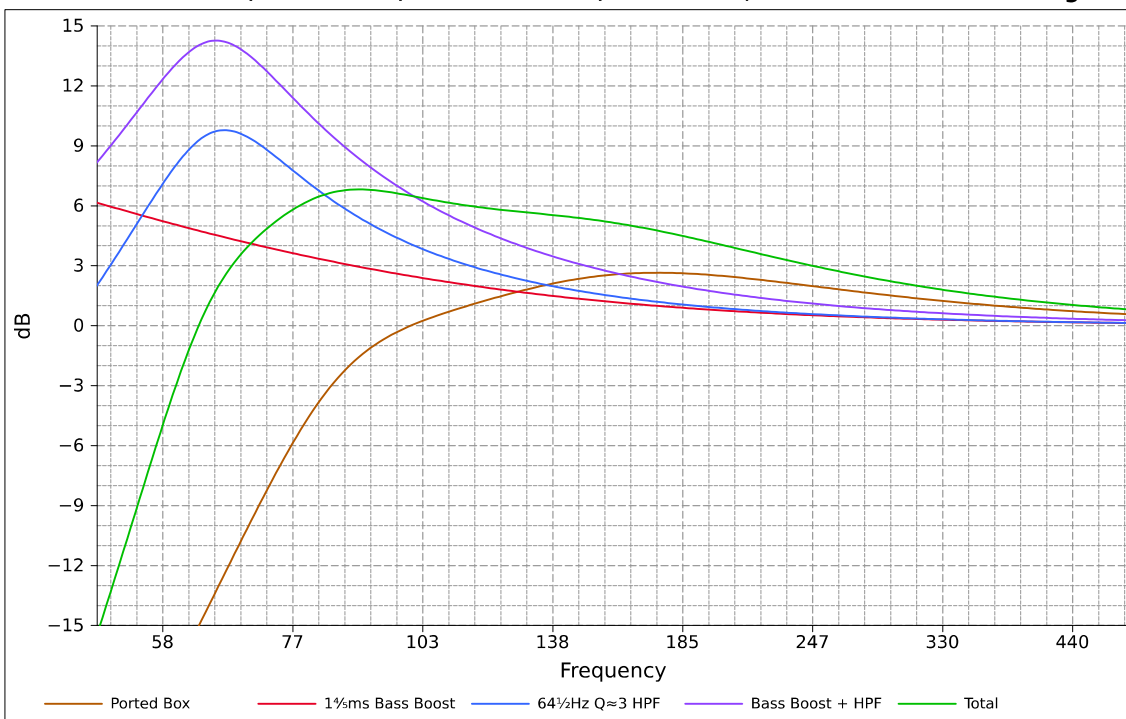**GRS 4½" 4FR-8, 225in³ Box, 2 Ports: 100Hz, ¾" PVC/20, 2.35cm I.D. × 5½cm Long**




The oscillator is fed through a current mirror and is also a current multiplier which allows the oscillator to operate at optimal current levels. It is possible to feed the oscillator directly if the supply voltage was higher but at 6V this provides the best overall solution.


The balanced mixer output is fed into an IF transformer and the secondary feeds a  $\pm 12\frac{1}{2}$ kHz ceramic filter. Its output feeds the AGC amp that uses a differential pair which varies the current division between the two thus providing a variable gain control. Its output feeds a high Q tank which performs a  $\pm 50\mu$ s de-emphasis ( $\pm 3.183$ kHz). This is advantageous for envelope detectors since wide bandwidths under marginal conditions causes the detector to greatly degrade. This signal also feeds the MC13028 AM Stereo Decoder, which also uses envelope detection, and for best separation must be precisely tuned. It will not be perfect but will only produce negligible separation loss. The rest of the de-emphasis is done after detection to produce the final NRSC 75 $\mu$ s w/8.7kHz pole response. It would be ideal to use a  $\pm 75\mu$ s ( $\pm 2.122$ kHz) IF response but the tank Q would be  $\sim 110$  and much harder to realize. With  $\pm 50\mu$ s the Q is  $\sim 71$  and easier to obtain with available components. While the Quasi-Sync™ regeneration detector will

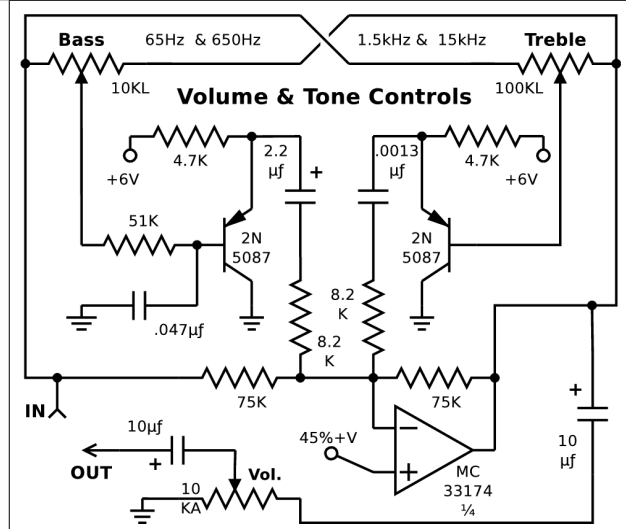

perform similar to a true synchronous detector with wide bandwidths this produces a 12dB/Oct. sideband attenuation above  $\pm 50\mu\text{s}$  ( $\pm 3.183\text{kHz}$ ) offering improved BFO protection. If the regeneration amp has a bandwidth of  $\pm 150\text{Hz}$  then its response at  $\pm 10\text{kHz}$  is  $-36.35\text{dB}$ . For the  $\pm 3.183\text{kHz}$  bandwidth its response at  $10\text{kHz}$  is  $-9.91\text{dB}$ . This is a total attenuation of  $-46.26\text{dB}$  offering very good BFO protection from adjacent channel carriers. However co-channel interference will depend on the capture ratio of the detector since the switch mode operation of the upper transistors in the Gilbert cell limits the signal. In the U.S.  $75\mu\text{s}$  is popular for audio but in other countries  $50\mu\text{s}$  is used.  $50\mu\text{s}$  also produces an  $\sim 10\text{dB}$  response like the NRSC emphasis curve, only the 2-3kHz corner difference range exists. Adding a Bass de-emphasis of  $2.65\text{ms}$  w/180Hz pole will add more headroom for the rest of the signal. Reducing Bass levels in transmission is of little consequence since they are less critical and degradation near the carrier and is well protected. The  $50\mu\text{s}$  &  $2.65\text{ms}$  w/180Hz pole curve would be a better standard to adopt, shown in the graph to the right.

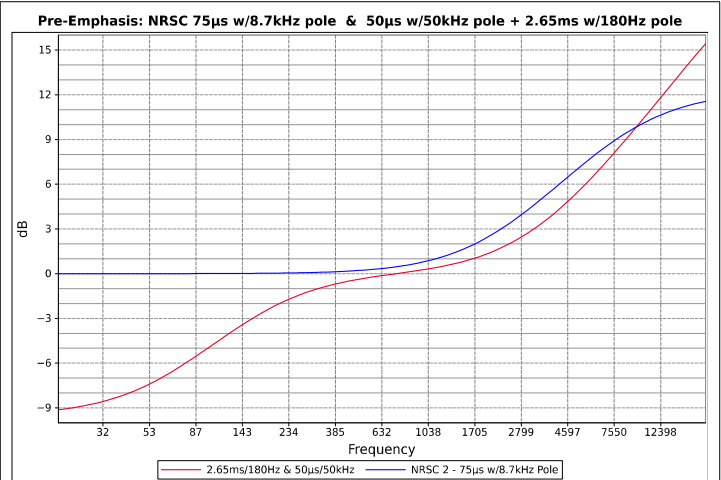

Adding to the NRSC equalization block in the receiver some high frequency equalization will be necessary to produce a flat  $-3\text{dB}@12\frac{1}{2}\text{kHz}$  response. Given the antenna bandwidth in wide mode and the ceramic filter attenuation a boost up to  $+6\text{dB}$  may be necessary. A  $12\frac{1}{2}\text{kHz}$  Chebyshev low pass filter with a Q of 2 can be used. Frequency response testing may be necessary to get it accurate.

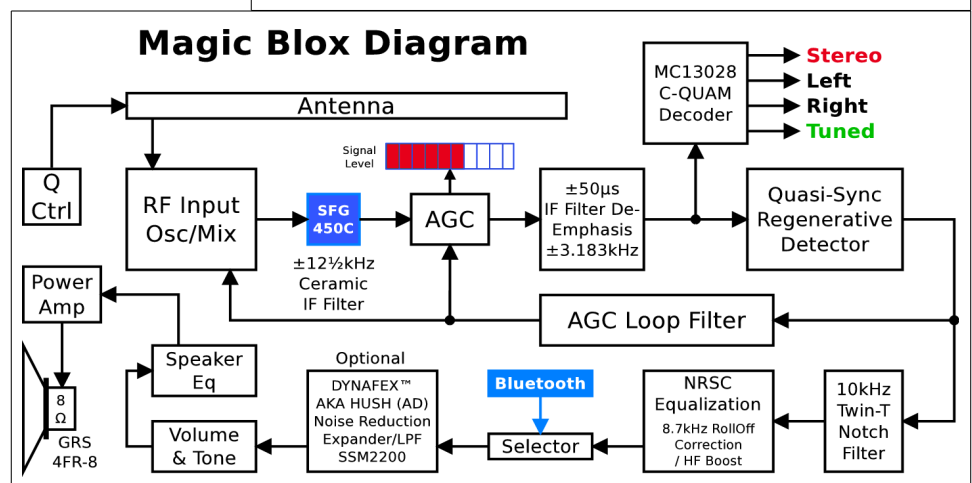


A portable speaker box with **Bluetooth** for connecting phones, tablets, or computers would be a benefit so adding this increases versatility.

In the 80's many car radios came with **DNR®**, a dynamic low loss filter, that provided noise reduction. Back then **DYNAFEX™** also produced the **SSM2200** chip that combined  $\sim 1\frac{1}{4}$  expansion with the this type of filter which provided up to 30dB of noise reduction. Today this circuit can be found in the **Analog Devices** chip **SSM2000** called the **HUSH Stereo Noise Reduction System**. It appears that **AD** may have bought out DYNAFEX and provides a dual channel version but may not make the single channel one now. This kind of noise reduction is ideal for AM since the broadcast signal is usually highly compressed and could stand expansion levels  $> 1\frac{1}{4}$  applied at the receiver.

The output amp uses a step up auto-transformer to produce the power from a 6V supply. This setup transforms the amplifier's impedance of  $2\Omega$  to the speakers  $8\Omega$  to get to this output level. The only other way to get this level of power output is to use a  $2\Omega$  speaker driven by a balanced output. To get 7W output the amp should use a 7V supply.

The available speaker chosen is the **GRS 4FR-8 4 $\frac{1}{2}$ "** and it is rated at 15W RMS with a frequency response of 100Hz - 10kHz and an 89dB SPL. It is touted as a replacement for the **Pioneer A11EC80-02F** which has a greater frequency response of 60Hz - 15kHz with a 96dB SPL. The Pioneer unit looks like a clone of the old **CTS 4 $\frac{1}{2}$ "** midrange that was used in the **Bose 901** speakers in a low  $\Omega$  version. The Pioneer unit looks like the better one to use or even the old CTS ones if either are available. Regardless of the one used all need equalization to flatten the response just like the Bose 901 and its custom equalizer to match. For the GRS a  $1\frac{1}{2}\text{ms}$  Bass Boost in the power amp's feedback and a  $64\frac{1}{2}\text{Hz}$   $Q \approx 3$  Chebyshev CVCS High Pass Filter ( $2 \times 0.15\mu\text{f}$ , 2.7K, 100K) should work in this ported WinISD designed box and at the high end a  $12\frac{1}{2}\text{kHz}$   $Q \approx 4\frac{1}{2}$  Chebyshev CVCS Low Pass Filter ( $2 \times 22\text{K}$ , 4.7nf, 68pf) is a starting point. This

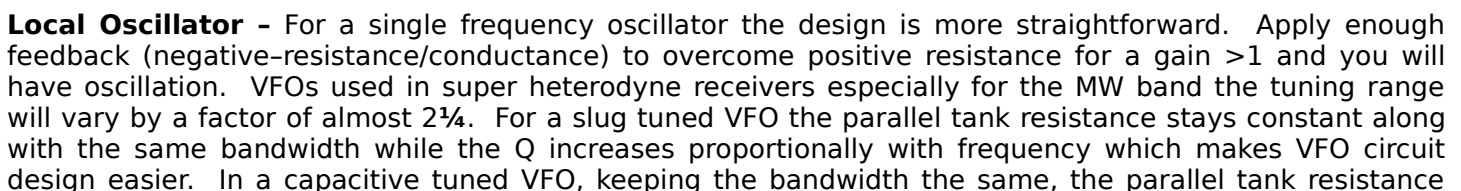

A current controlled variable input supply produces a proportional modulated output current level which in this circuit controls mixer gain for the AGC. However for capacitive tuned setups an increase in supply current increases Vp-p levels and from low to high frequency the increase is mostly proportional. At the high end and maximum AGC current maximum p-p levels will occur and must be limited to work within circuit boundaries. The amount of feedback needed is greater at the low end so supplying just enough at minimum current levels is critical and at the top end its more than adequate for oscillation and can be overkill if not chosen properly. It may be possible to use a small inductor to decrease feedback as frequency increases to partially compensate for this. The **E**mitter to feedback tap ratio should be chosen to produce enough load to match the drive current provided by the transistor for operation within circuit p-p boundaries. The tap connected to the **B**ase should be ~18% greater than the other to supply an over unity gain for reliable feedback. Feedback can then be reduced via a resistor for optimization. This 18% value is for fixed gain single frequency but for VFO+Gain this could need to be as high as 45%.

[illegible]

### Filtering for GRS 4FR-8 4½" Speaker

The image shows two circuit diagrams for a GRS 4FR-8 4½" speaker. The left diagram is a High Pass Filter with a 64½ Hz Q ≈ 3 Chebyshev response. It consists of a .15µf capacitor in series with the input, followed by a 2.7K resistor in parallel with the feedback path of an op-amp. A 100K resistor is connected from the non-inverting input to ground. The right diagram is a Low Pass Filter with a 12½ kHz Q ≈ 4% Chebyshev response. It consists of a 22K resistor in series with the input, followed by a .0047µf capacitor in parallel with the feedback path of an op-amp. A 100pf capacitor is connected from the non-inverting input to ground.

**GRS 4½" 4FR-8, 4.8L Box, 2 Ports: 80Hz, ¾" PVC/20, 2.35cm I.D. × 6½cm Long**

